

BCA 108 N

B.C.A. (PART-I) EXAMINATION, 2024-25

(SECOND SEMESTER)

Paper : III

(New Course)

Digital Circuit and Logic Design

Time : Three Hours]

[Maximum Marks : 75

- Note:** (i) Answer **Five** Questions in all.
(ii) Question No.-1 is **Compulsory**.
(iii) Answer remaining **four** questions, selecting **two** questions from each Section A and B.
(iv) All questions carry equal marks.

1. Answer all parts of the following :
- Design and draw the logic diagram of full adder.
 - What is flip-flop ? Explain.
 - State the Boolean distributive law.
 - What is register ? Explain
 - What is multiplexers ?

Section-A

2. Give difference between the following:
- SRAM vs DRAM
 - Register vs Counters

5801



3. Discuss various types of Logic Gates. Also discuss their applications.
4. Draw the master slave JK flip-flop and explain its working.
5. What is Karnaugh Map ? Explain 4-variable K-map with an example.

Section-B

6.
 - (a) Differentiate between asynchronous and synchronous counters.
 - (b) Design and explain a half subtractor with truth table and circuit.
7.
 - (a) Convert the following :
 - (i) $(1101010)_2$ to hexadecimal
 - (ii) $(2F)_{16}$ to decimal
 - (iii) $(1101011)_2$ to Octal
 - (b) Explain the working of full adder with logic diagram and truth table.
8.
 - (a) Explain SOP and POS forms with example.
 - (b) Differentiate between combinational and sequential circuits.
9. Write notes on any two of the following:
 - (a) Encoder and Decoder
 - (b) Maxterm and Minterm
 - (c) Cache Memory

